

---

# [SoC Design] HW Design for FFT (Lab2)

Chester Sungchung Park (박성정)  
SoC Design Lab, Konkuk University  
Webpage: <http://soclub.konkuk.ac.kr>

# Outline

---

- ❑ Objectives
- ❑ Hardware architecture for FFT
  - Single-path delay feedback (SDF)
- ❑ Lab 2: H/W Design

# Objectives

---

- ❑ After completing this lab, you will be able to:
  - Create a Vivado RTL project
  - Synthesize the RTL project
  - Implement the RTL project
  - Run Behavioral / Post-Synthesis simulations

# Hardware Architecture for FFT


---

- ❑ Parallel architectures
  - No-brainer implementation
- ❑ Pipeline architectures
  - Single-path Delay Feedback (SDF)

# Parallel Architecture
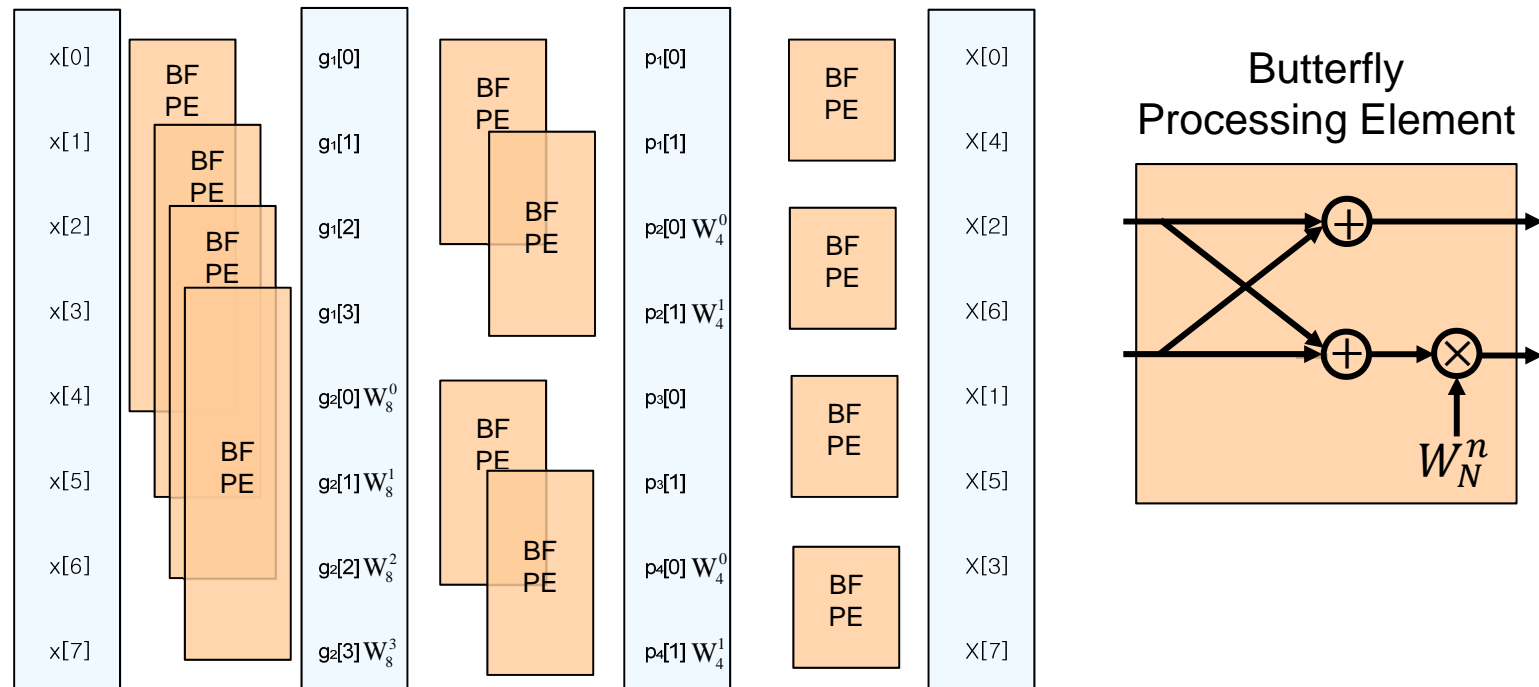
## □ Block diagram


- Totally  $N/2$  butterfly processing elements per stage
- Example: 8-pt FFT ( $N = 8$ )



# Parallel Architecture
 
## □ Performance metrics

- Latency:  $(N + \log_2 N)T_{clk} [sec]$   
✓ Reordering ignored
- Throughput:  $1/T_{clk} [samples/sec]$
- Example: 8-pt FFT ( $N = 8$ )



# Parallel Architecture

## □ Complexity metrics: S/W case

- No. of instruction cycles

```
for (data=0;data<N;data++) {  
    input[data].real_no=in_re[data];  
    input[data].img_no=in_im[data];  
}
```

Input Loading

```
for (n=0;n<32;n++) {  
    temp[n]=add_cal2(input[n],input[n+32]);  
    temp[n+32]=multiple2(sub_cal2(input[n],input[n+32]),W2[n]);  
    temp[n+32].real_no /= TW_factor;  
    temp[n+32].img_no /= TW_factor;  
}
```

Stage #1

.....

```
for(n=0;n<32;n++) {  
    input[(2*n)]=add_cal2(temp[(2*n)],temp[(2*n)+1]);  
    input[(2*n)+1]=sub_cal2(temp[(2*n)],temp[(2*n)+1]);  
}
```

Stage #6

```
for(n=0;n<N;n++) {  
    X[n]=input[bit_revesal(n)];  
}  
for(n=0;n<N;n++) {  
    out_re[n] = X[n].real_no;  
    out_im[n] = X[n].img_no;  
}
```

Reordering  
+ Output Loading

## S/W Profiling (Cortex-A9)


Functions	Execution Time	
	usec	%
Input	3.7	5.2
Stage #1	9.0	12.6
Stage #2	10.7	15.0
Stage #3	10.5	14.7
Stage #4	10.5	14.7
Stage #5	10.5	14.6
Stage #6	5.2	7.3
Reordering + Output	11.5	16.1
<b>Total</b>	<b>71.7</b>	<b>100</b>

# Parallel Architecture

## □ Complexity metrics: H/W case

- Area

	BF-PE	Register
4	4	8
8	12	24
16	32	64
64	192	384
$N$	$(N/2) \log_2 N$	$N \log_2 N$

 



Necessary to reduce No. of BF PEs  
In order to reduce complexity (area)



# Single-Path Delay Feedback
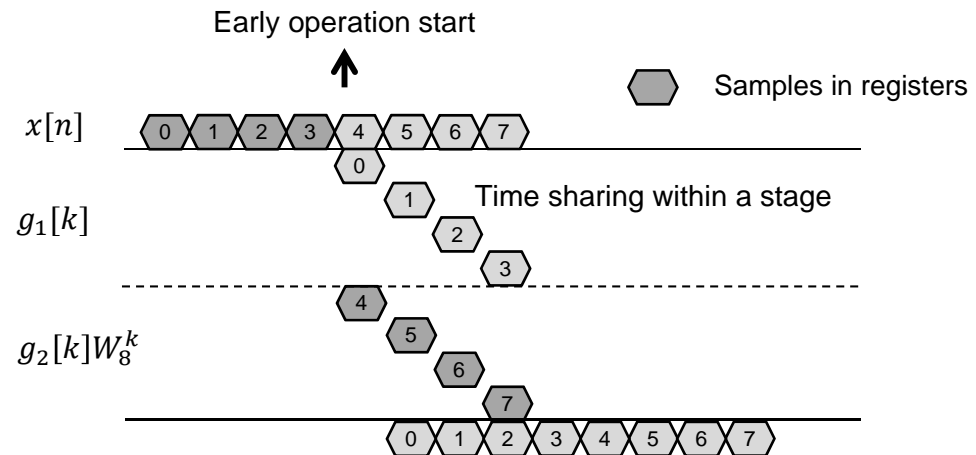 
## □ Pipeline architecture


- Efficient use of BF-PE
  - ✓ Time sharing within a stage
  - ✓ Early operation start
- Example: 8-pt FFT ( $N = 8$ )




# Single-Path Delay Feedback
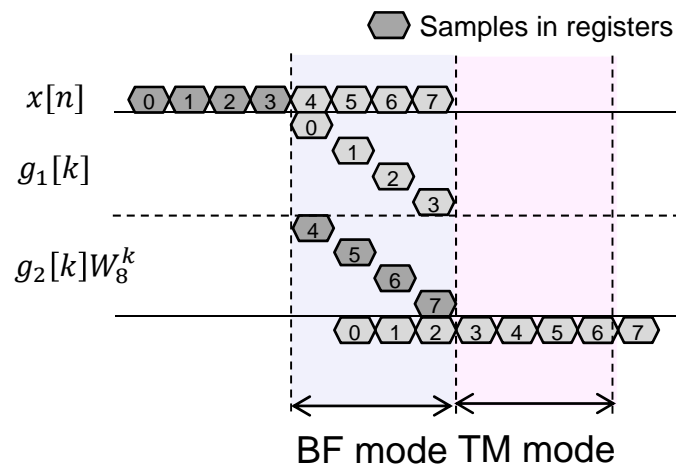
## □ Block diagram


- One BF-PE + fewer registers per stage
- Switching btw. BF/TM modes
- Example: 8-pt FFT ( $N = 8$ )



BF mode

 


TM mode

 

# Single-Path Delay Feedback

## □ Block diagram

- Example: 8-pt FFT ( $N = 8$ )


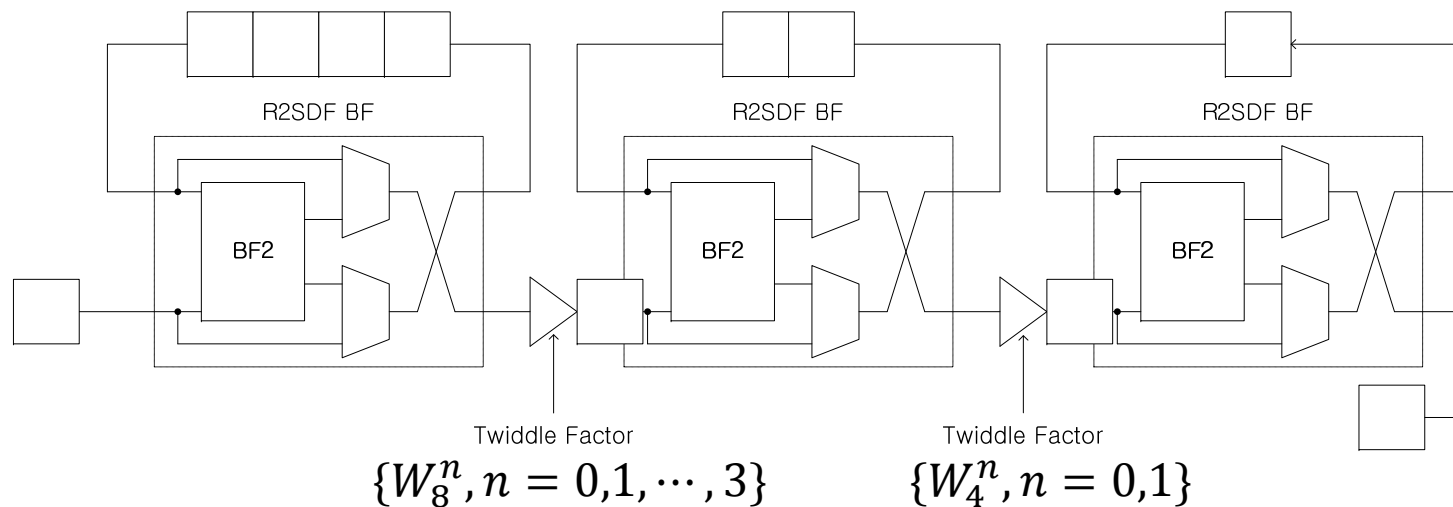


[E. H.Wold et al., IEEE T-Computer, 1984 ]

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 0

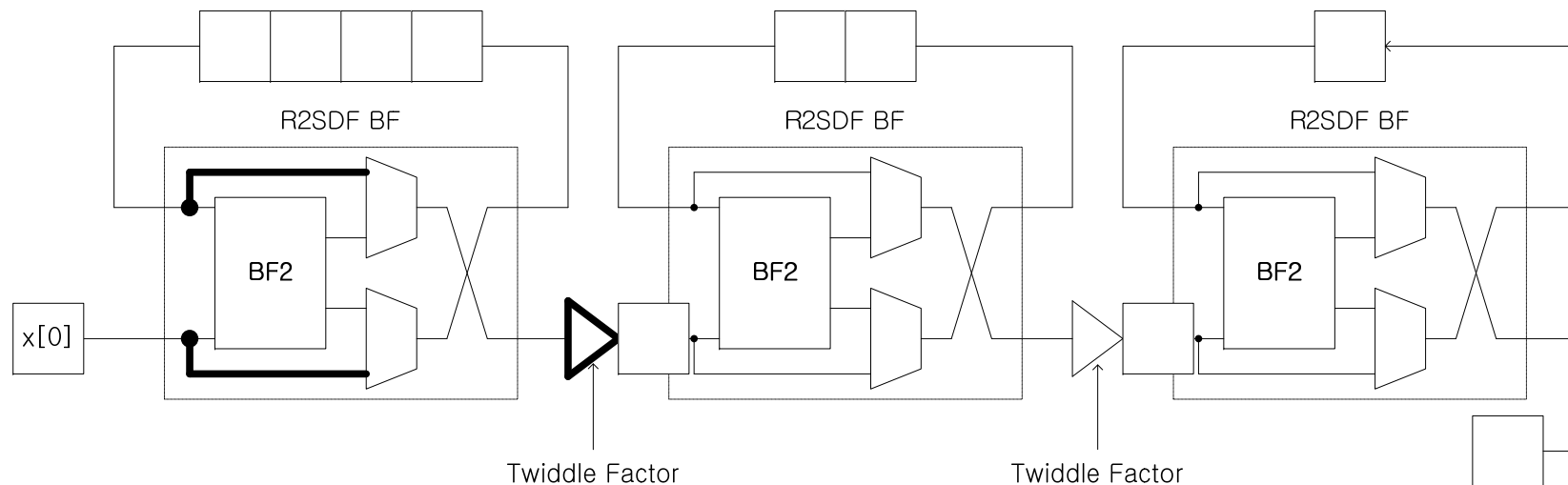 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 1

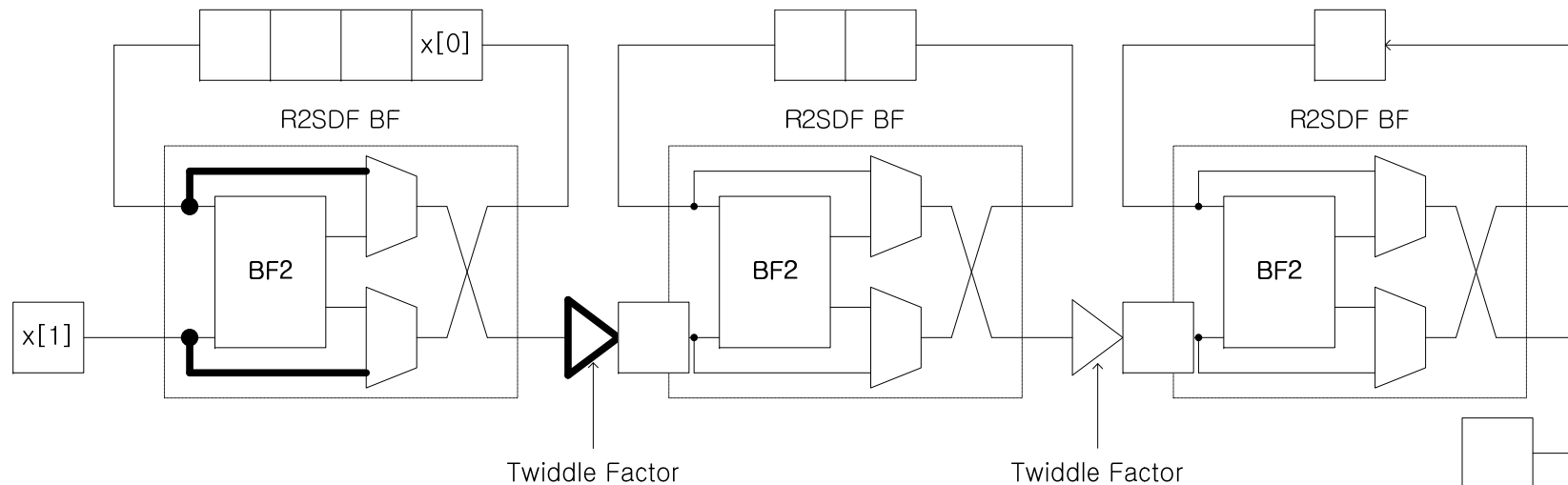 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 2

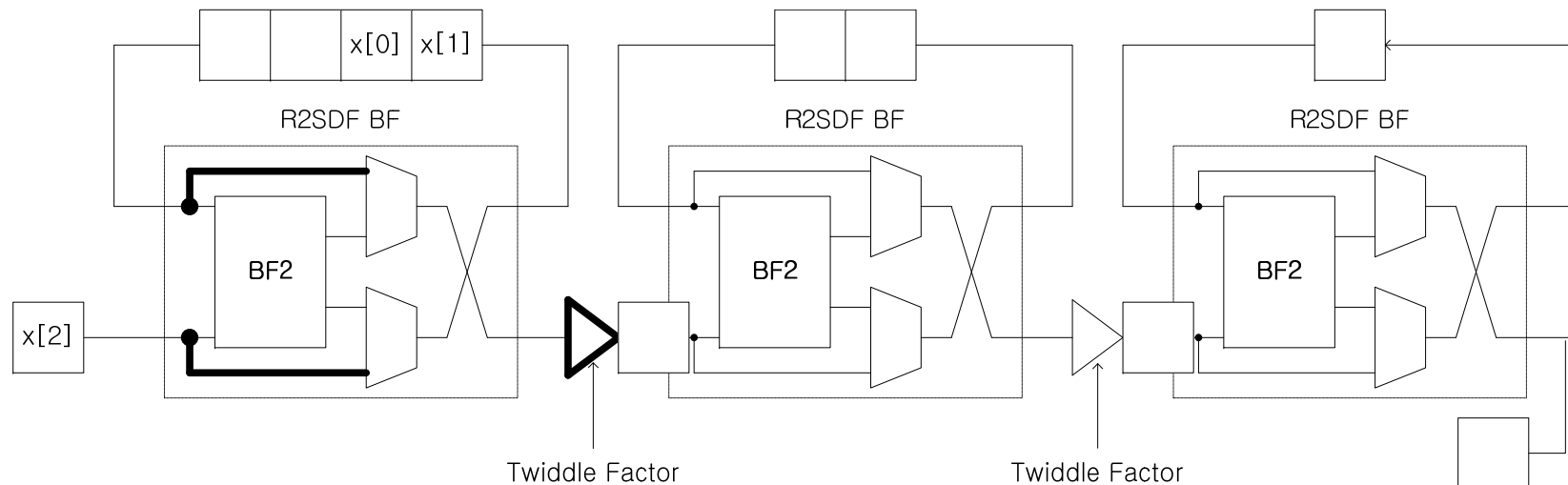 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 3

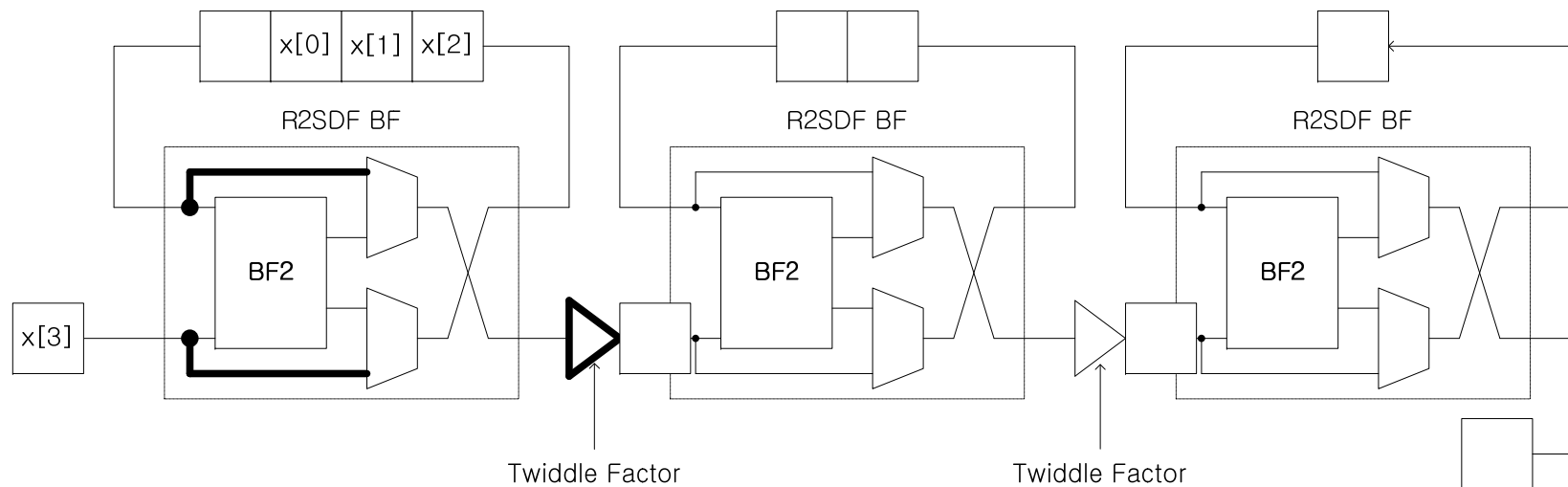 

# Single-Path Delay Feedback

## □ Pipeline operation

- Clock cycle 4

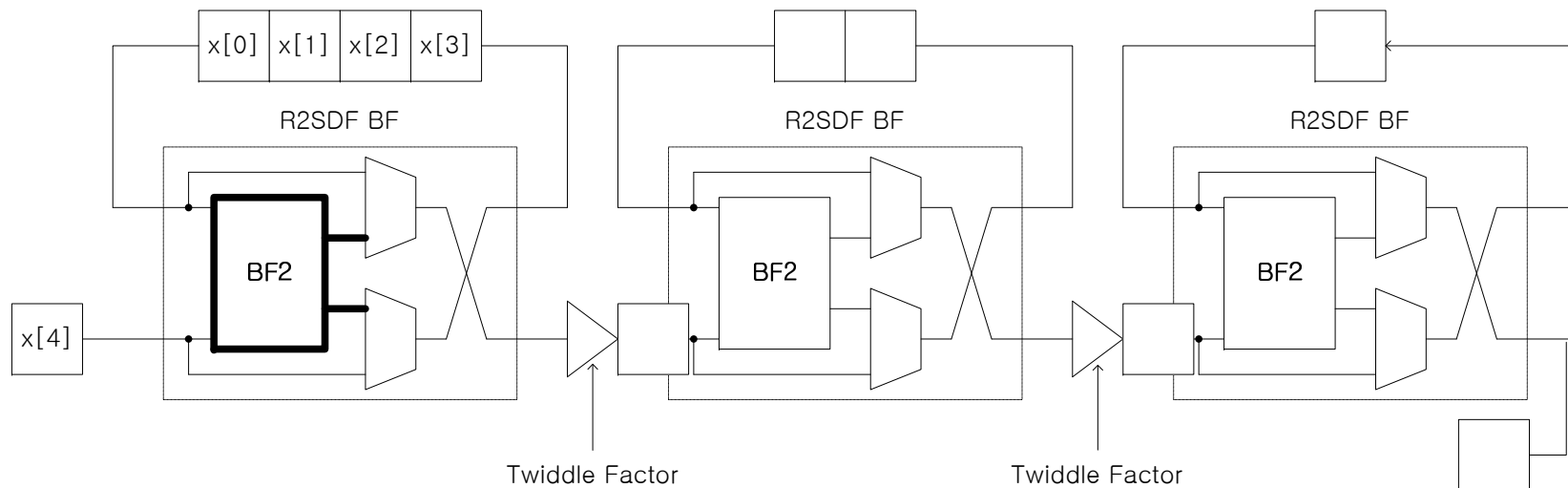
 




# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 5

 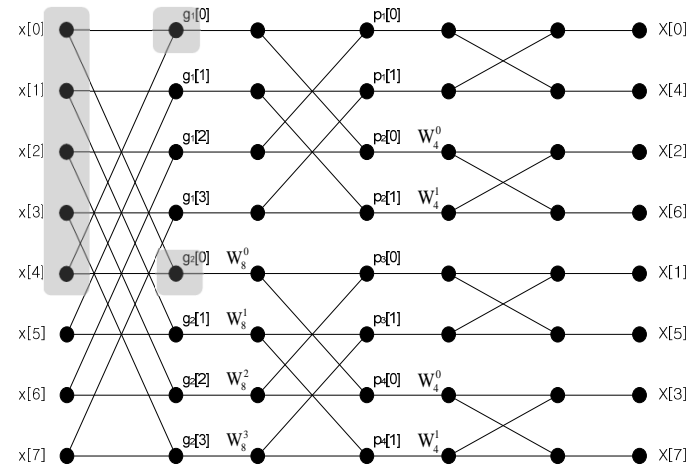

# Single-Path Delay Feedback



## □ Pipeline operation

- Clock cycle 6

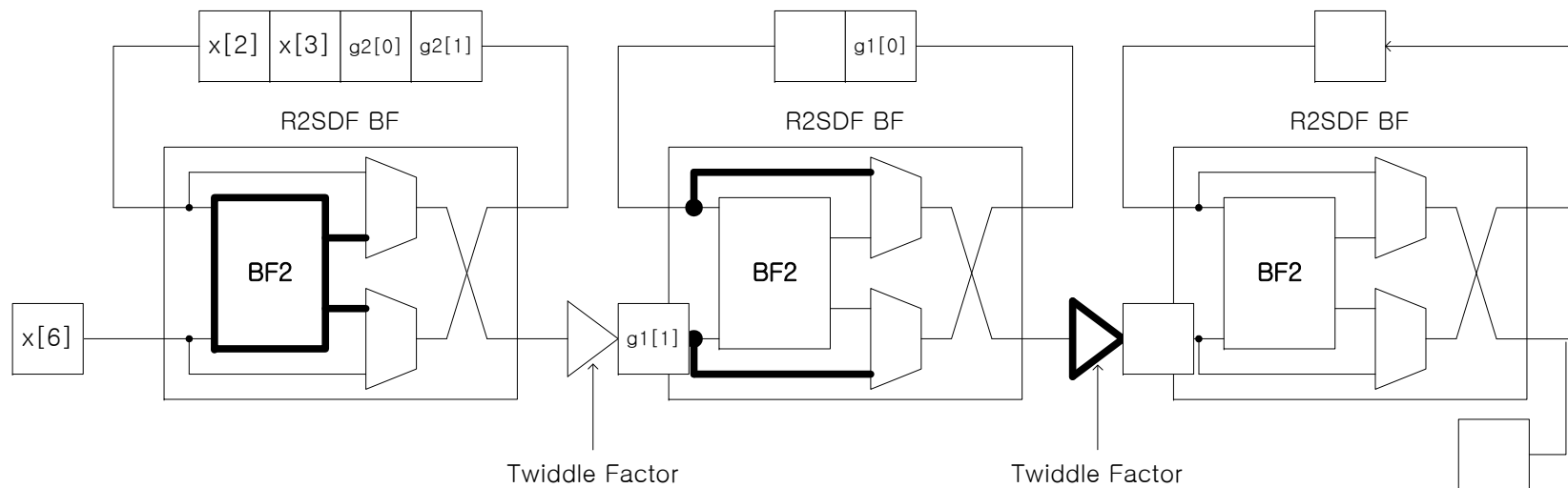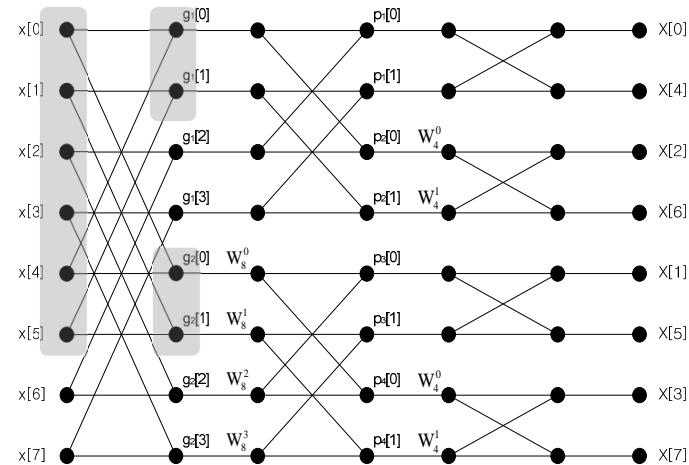

# Single-Path Delay Feedback



- Pipeline operation
  - Clock cycle 7

 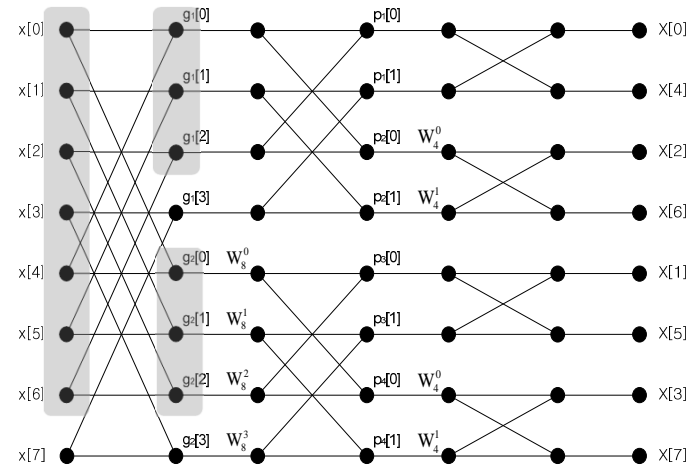

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 8

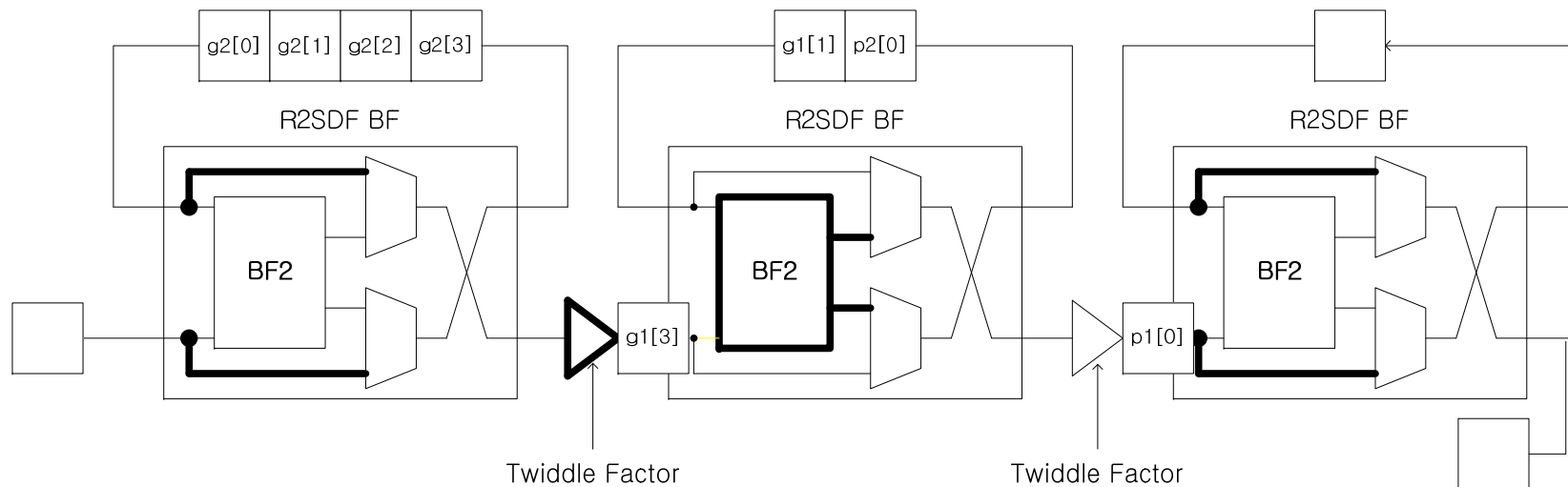 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 9

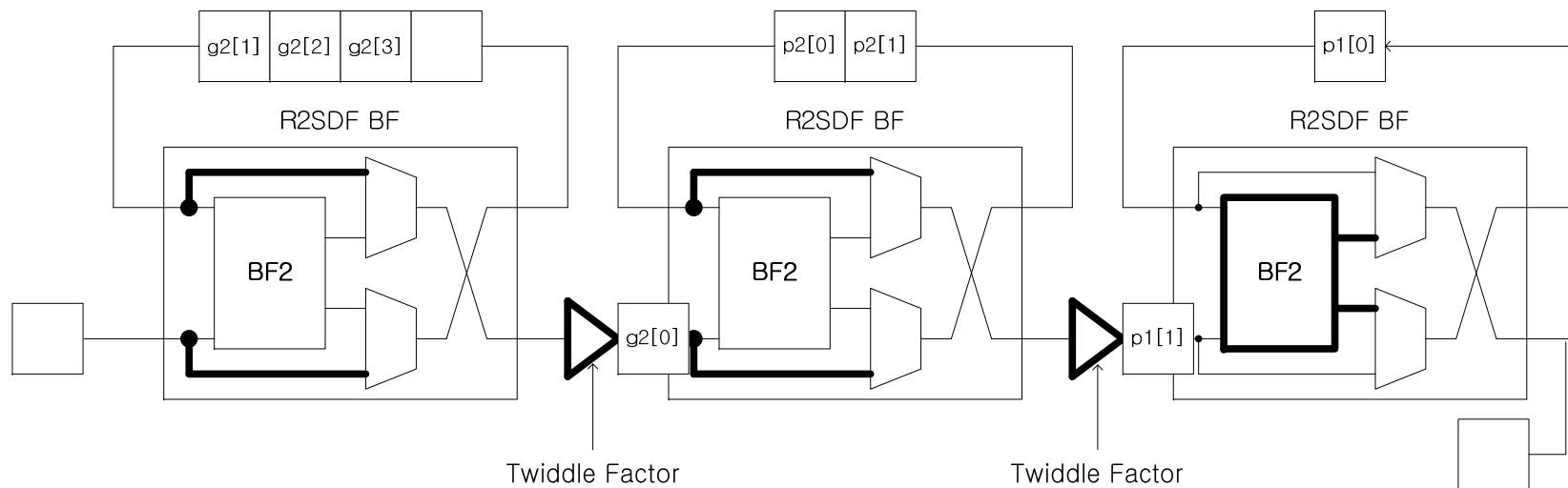 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 10

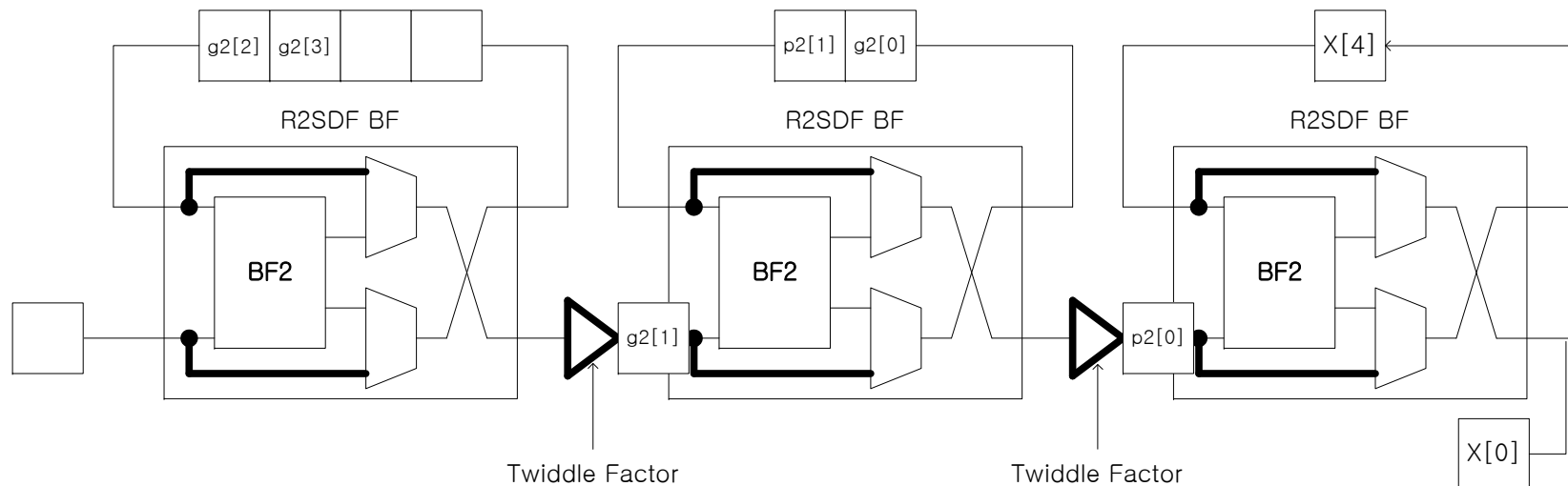 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 11

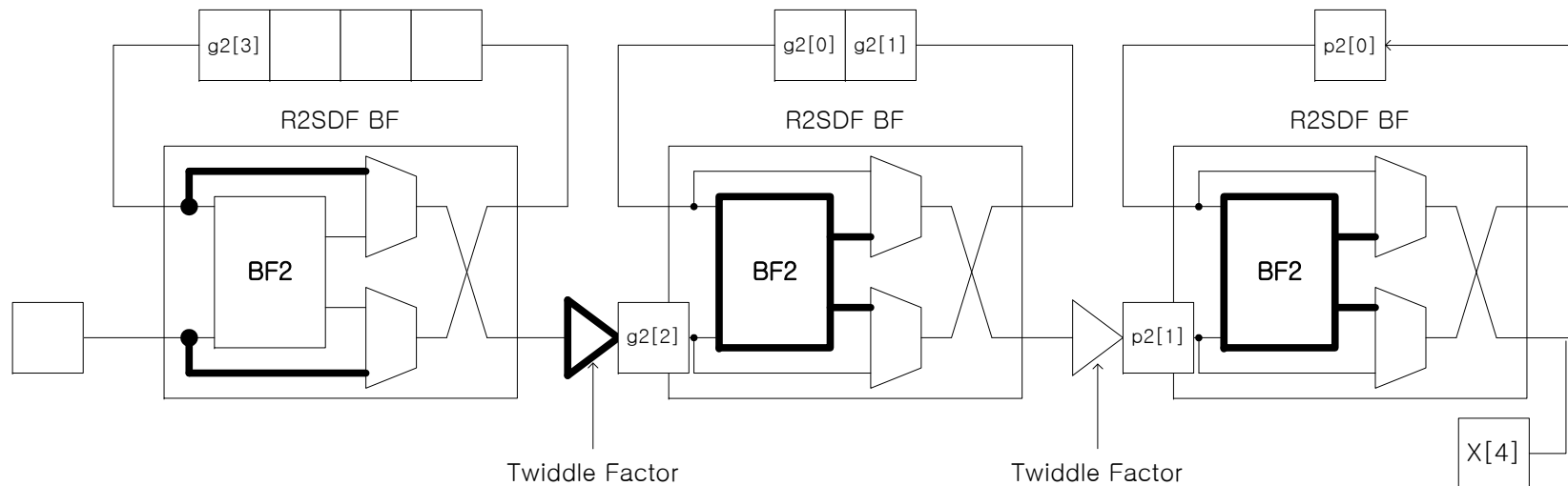 

# Single-Path Delay Feedback

## □ Pipeline operation

- Clock cycle 12

 
 




# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 13

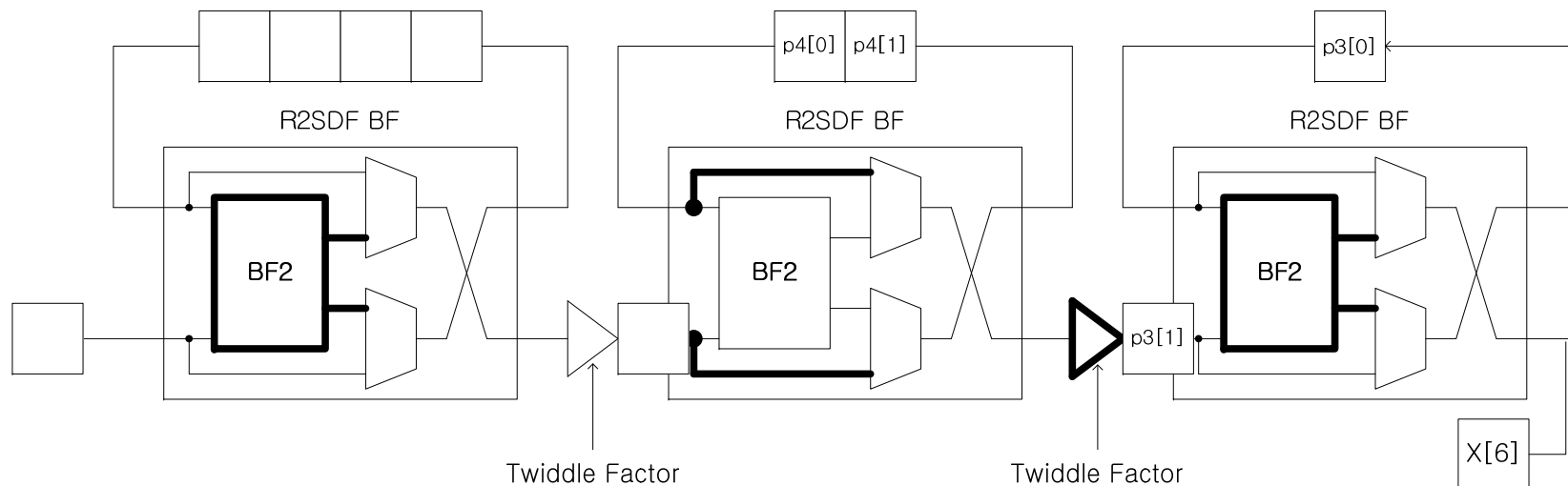 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 14

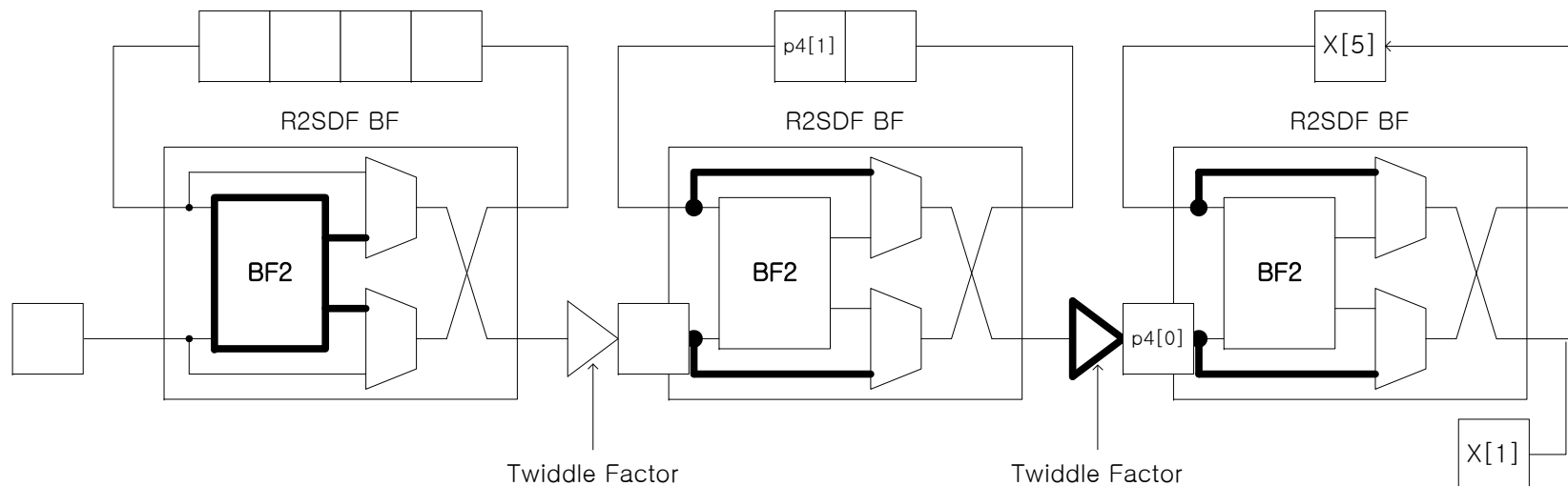 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 15

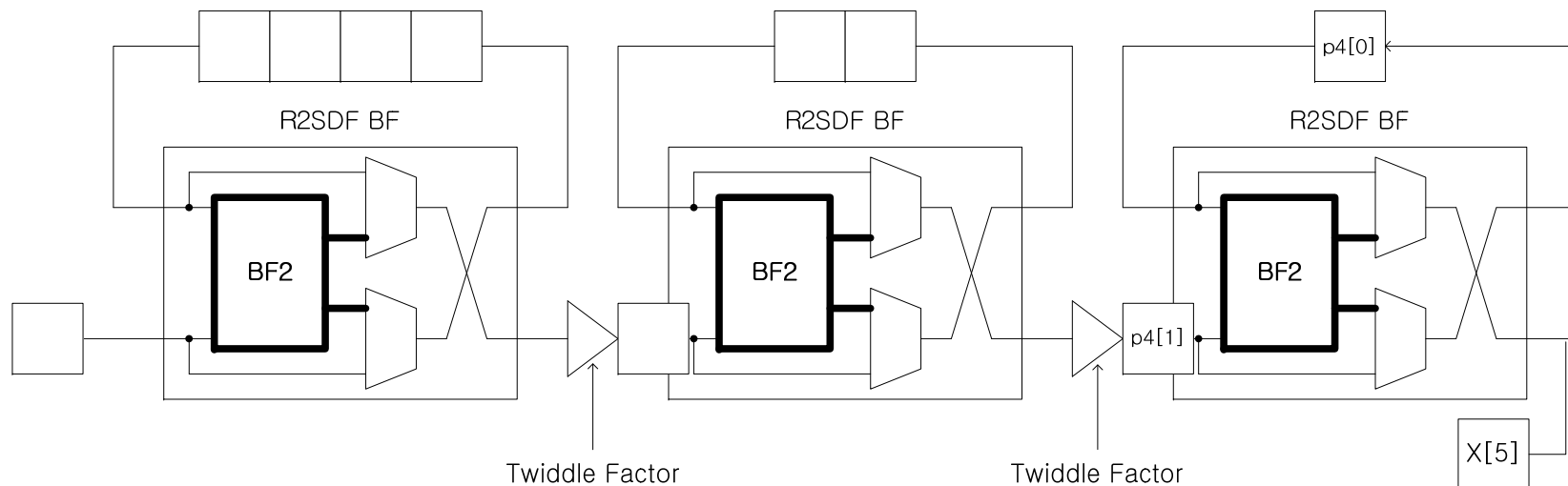 

# Single-Path Delay Feedback

## □ Pipeline operation



- Clock cycle 16

  

# Single-Path Delay Feedback

## □ Pipeline operation


- Clock cycle 17

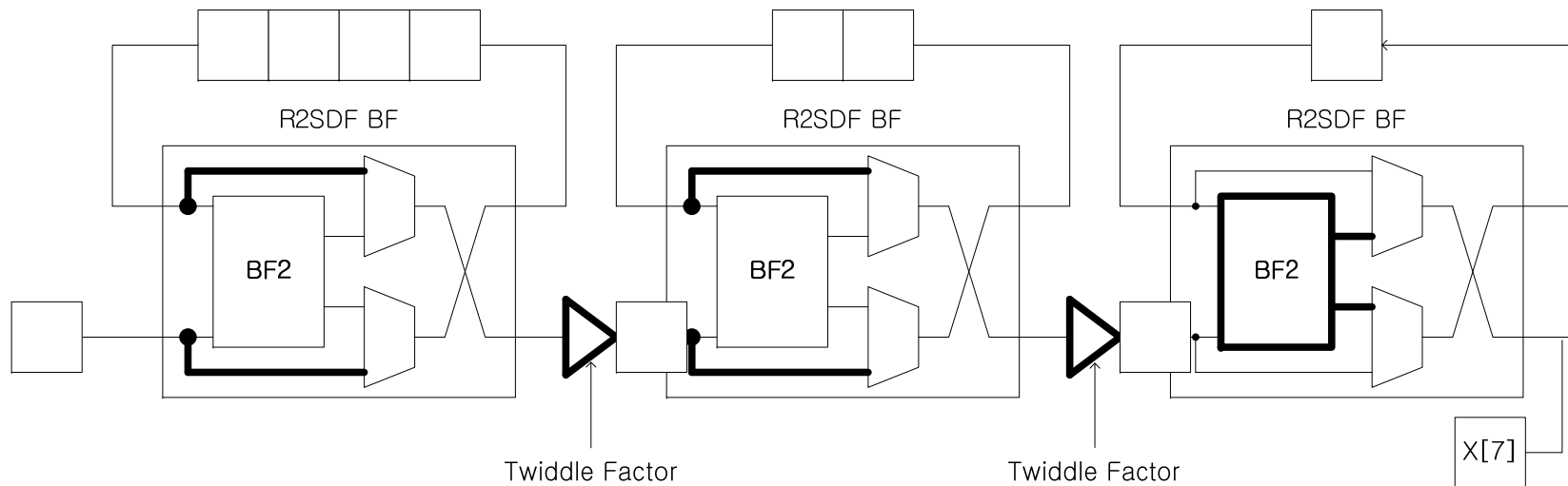 

# Single-Path Delay Feedback
 
## □ Performance metrics

- Latency:  $((N - 1) + \log_2 N)T_{clk} [sec]$
- Throughput:  $1/T_{clk} [samples/sec]$
- Example: 8-pt FFT ( $N = 8$ )



H/W utilization rate:

- BF: 50%
- Register: 100%

# Single-Path Delay Feedback

## □ Complexity metrics

- Area: Comparison with parallel architecture


	Parallel		Pipeline	
	BF-PE	Register	BF-PE	Register
4	4	8	2	5
8	12	24	3	10
16	32	64	4	19
64	192	384	6	69
$N$	$(N/2) \log_2 N$	$N \log_2 N$	$\log_2 N$	$(N - 1) + \log_2 N$

Complexity reduction by  $\sim \frac{2}{N}$  !

# Single-Path Delay Feedback

## □ Complexity metrics

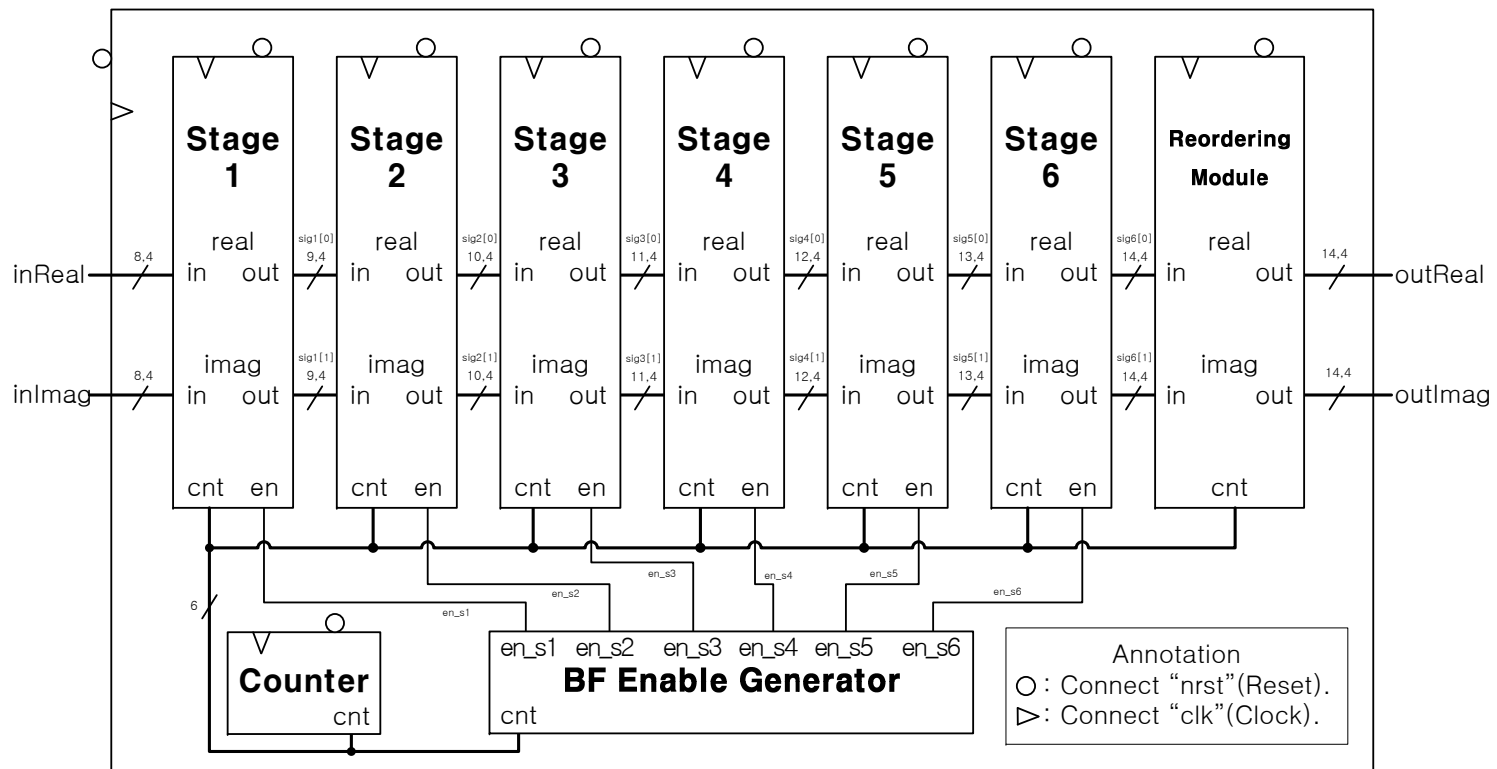- Example: 64-pt Radix-2 SDF (CMOS 180nm)




Courtesy: S.W. Kim and J. H. Wang, Konkuk Univ.



# Single-Path Delay Feedback

## □ Complexity metrics (cont'd)

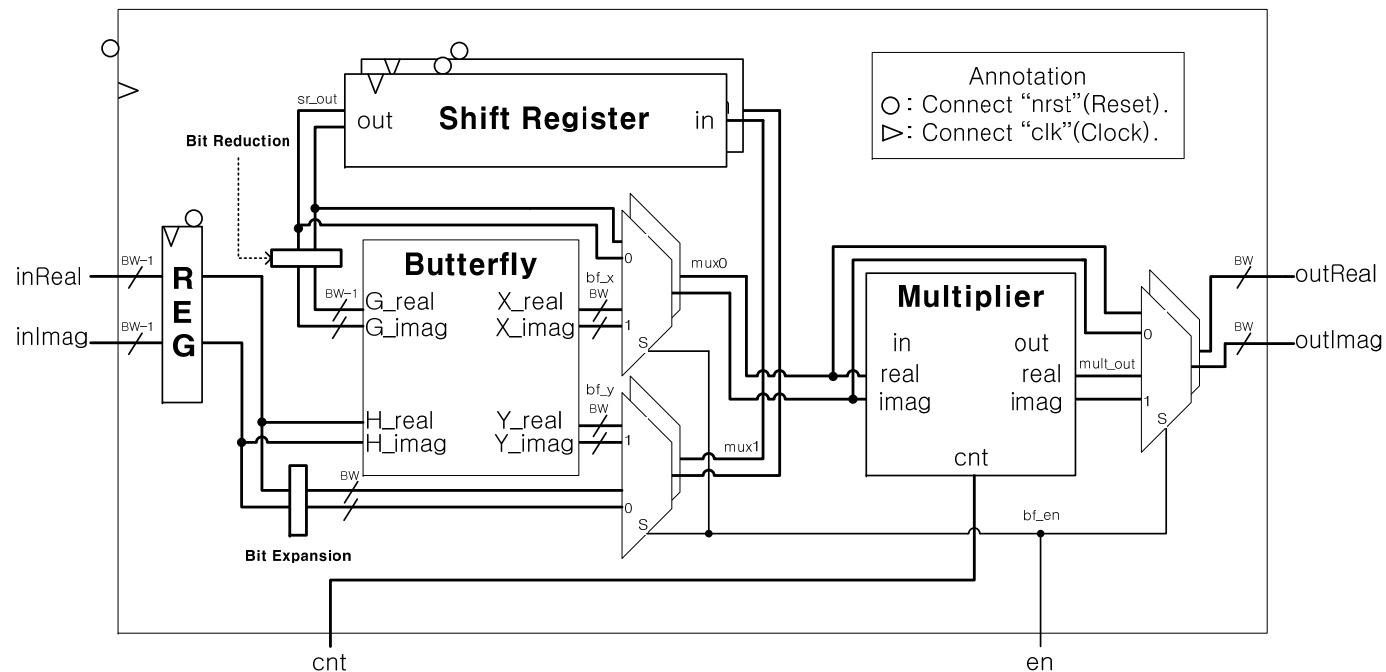- Example: 64-pt Radix-2 SDF (CMOS 180nm)



Courtesy: S.W. Kim and J. H. Wang, Konkuk Univ.

# Single-Path Delay Feedback

## □ Complexity metrics (cont'd)

- Example: 64-pt Radix-2 SDF (CMOS 180nm)


Area (um <sup>2</sup> )						
	Stage1	Stage2	Stage3	Stage4	Stage5	Stage6
Butterfly	3632	3925	4217	42031	4803	5096
Multiplier	33430	34907	35339	25995	4617	-
Shift Reg0	23923	12799	6819	3639	1922	-
Shift Reg1	23923	12799	6845	3639	1922	-
Stage Area	88314	68123	57196	42031	17769	11688
RvReg	392875					
Cnt	592					
Total Area	679000 (Stage1+..+Stage6+RvReg+Cnt)					

Courtesy: S.W. Kim and J. H. Wang, Konkuk Univ.

# Fixed-Point Arithmetic
 
## □ Full-precision BF-PE

- Equal word length assumed for real & imaginary parts
  - ✓  $x_r[p], x_i[p], x_r[q], x_i[q] \sim [1, N_x], W_{Nr}^n, W_{Ni}^n \sim [1, N_w]$
- **Neither quantization nor overflow** allowed
  - ✓  $X_r[p], X_i[p] \sim [2, \max(N_x, N_w)]$
  - ✓  $X_r[q], X_i[q] \sim [2, \max(N_x, N_w) + N_w]$




- Word length expansion
  - ✓ One extra integer bit + many extra fractional bits

# Fixed-Point Arithmetic
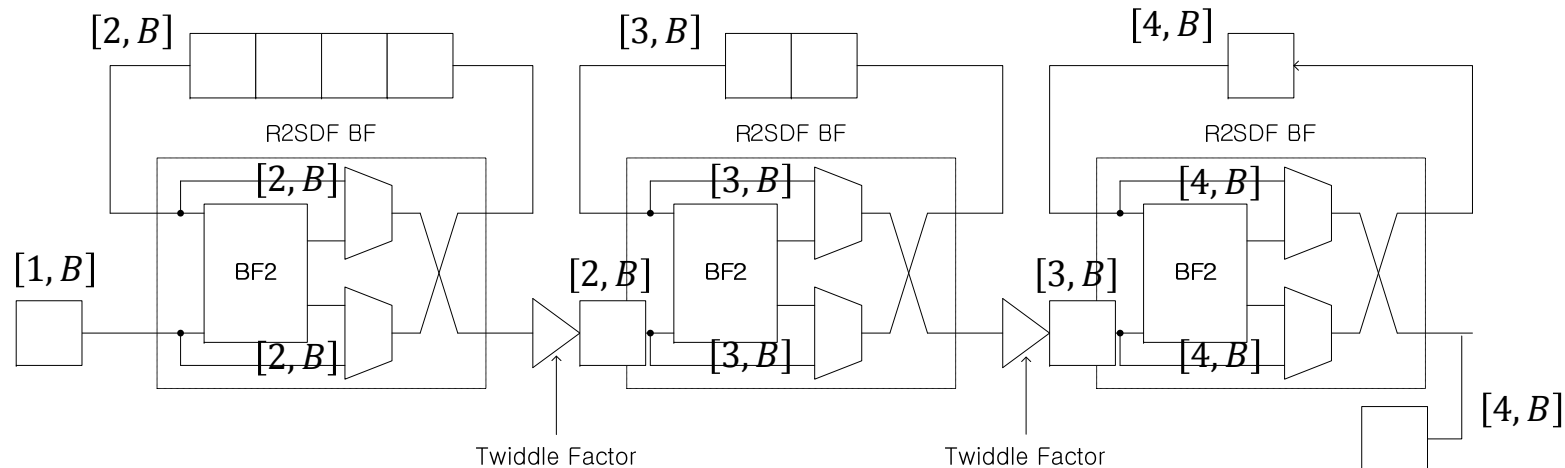
## □ Finite-WL BE-PE


- 1 bit expansion per stage in MSB → No overflow
- No expansion in LSB → Quantization
  - ✓  $X_r[p], X_i[p], X_r[q], X_i[q] \sim [2, \max(N_x, N_w)]$
- Example: 8-pt FFT ( $B = 8$ )
  - ✓  $N_x = N_w = B$



# Fixed-Point Arithmetic
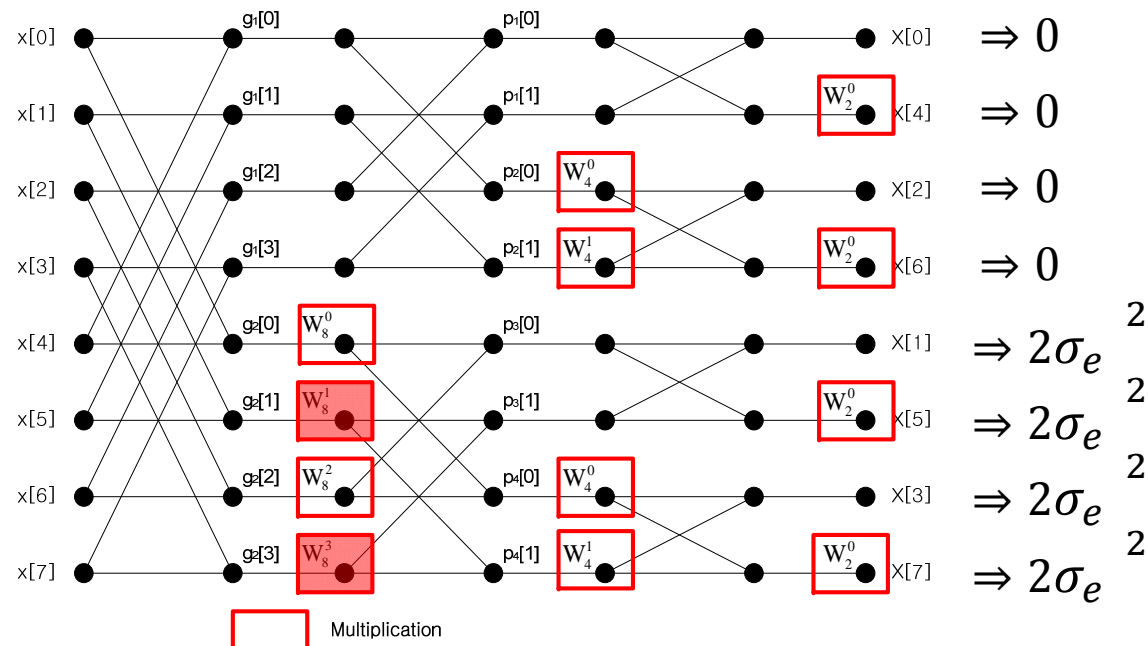
## Quantization error (rounding)


- Increase by  $\sigma_e^2 = \frac{2^{-2B}}{12}$  per (nontrivial constant) multiplication
- Example: 8-pt FFT ( $N = 8$ )



# Performance Metrics
 
## □ Quantization error


- Quantization-error-to-signal ratio:  $\frac{\sigma_e^2}{\sigma_s^2} = 4N \times 2^{-2B}$ 
  - ✓ Proportional to FFT size ( $N$ )
  - ✓ Exponential with word length ( $B$ ): -6 dB/bit



Courtesy: S.W. Kim, Konkuk Univ.

# Complexity Metrics

## □ Area (CMOS 180nm)

 


Courtesy: S.W. Kim and J. H. Wang, Konkuk Univ.

# Performance-Complexity Trade-off

## □ Area vs. Delay

- 64-pt Radix-2 SDF (CMOS 180nm)

 


Courtesy: S.W. Kim and J. H. Wang, Konkuk Univ.


 
# Performance-Complexity Trade-off

- Quantization error vs. Area (CMOS 180nm)
  - With respect to word length



Courtesy: S.W. Kim and J. H. Wang, Konkuk Univ.

# Lab 2: HW Design

---

- ☐ Creating RTL projects
- ☐ Programming in RTL
- ☐ Running Behavioral Simulation
- ☐ Running Synthesis
- ☐ Running Implementation

# Source Codes

## ❑ tb\_Top\_FFT.v

```
1 `timescale 1ns/1ps
2 `define p 2
3 module tb_Top_FFT;
4
5     reg nrst,clk;
6
7
8     reg [15:0] input_re[191:0];
9     reg [15:0] input_im[191:0];
10
11     reg [15:0] output_re[191:0];
12     reg [15:0] output_im[191:0];
13
14     wire [15:0] inReal,inImag;
15     wire [15:0] outReal,outImag;
16
17     integer clkcnt;
18
19     reg start;
20
21
22     Top_FFT top0(.nrst(nrst),.clk(clk),.start(start),.valid(1'b1),
23     |         .inReal(inReal),.inImag(inImag),
24     |         .outReal(outReal),.outImag(outImag));
25
26     always
27     |     #(`p/2) clk = !clk;
28
29     always@(negedge clk)
30     |     clkcnt = clkcnt +1;
31
```

```
32 initial begin
33     clk = 0;
34     nrst = 0;
35     clkcnt=-103;
36     start = 0;
37     $readmemb("binary_in_real.txt", input_re);
38     $readmemb("binary_in_imag.txt", input_im);
39
40     #(100*`p) start = 1'b1;
41     #(`p/2+1) nrst = 1;
42 end
43
44 assign inReal = clkcnt > -2? input_re[clkcnt+1] : 0;
45 assign inImag = clkcnt > -2? input_im[clkcnt+1] : 0;
46
47 always @ (posedge clk) begin
48     output_re[clkcnt+1] <= outReal;
49     output_im[clkcnt+1] <= outImag;
50 end
51
52
53 integer dumpfile, i;
54 initial begin
55
56
57     #(292*`p +1) dumpfile = $fopen("binary_out_real.txt","w");
58     for(i = 0; i<192;i=i+1)begin
59         $fwrite(dumpfile,"%b\n",output_re[i]);
60     end
61     $fclose(dumpfile);
62
63     dumpfile = $fopen("binary_out_imag.txt","w");
64     for(i = 0; i<192;i=i+1)begin
65         $fwrite(dumpfile,"%b\n",output_im[i]);
66     end
67     $fclose(dumpfile);
68
69     $stop;
70 end
71
72
73 endmodule
```

# Source Codes

## □ Top\_FFT.v

```
1  module Top_FFT #(
2      parameter in_BW = 16,
3      parameter out_BW= 22,
4      parameter cut_BW= 6
5  ) (
6      input nrst,clk,start,
7      input valid,
8      input [in_BW-1:0] inReal,inImag,
9      output[out_BW-cut_BW-1:0] outReal,outImag
10 );
11
12 wire [5:0] cnt;
13
14 wire [in_BW :0] sig1[1:0];
15 wire [in_BW+1:0] sig2[1:0];
16 wire [in_BW+2:0] sig3[1:0];
17 wire [in_BW+3:0] sig4[1:0];
18 wire [in_BW+4:0] sig5[1:0];
19 wire [in_BW+5:0] sig6[1:0];
20
21 wire en_s1,en_s5,en_s6;
22 reg en_s2;
23 reg [2:0] en_s4;
24 reg [1:0] en_s3;
25
26 Counter cnt0(nrst,clk,start, valid,cnt);
27 Stage #(in_BW+1,32) stage1(nrst,clk,en_s1,cnt,inReal,inImag, valid, sig1[0],sig1[1]);
28 Stage #(in_BW+2,16) stage2(nrst,clk,en_s2,cnt,sig1[0],sig1[1], valid, sig2[0],sig2[1]);
29 Stage #(in_BW+3,8 ) stage3(nrst,clk,en_s3[1],cnt,sig2[0],sig2[1], valid, sig3[0],sig3[1]);
30 Stage #(in_BW+4,4 ) stage4(nrst,clk,en_s4[2],cnt,sig3[0],sig3[1], valid, sig4[0],sig4[1]);
31 Stage #(in_BW+5,2 ) stage5(nrst,clk,en_s5,cnt,sig4[0],sig4[1], valid, sig5[0],sig5[1]);
32 Stage6 #(in_BW+6,1 ) stage6(nrst,clk,en_s6 ,sig5[0],sig5[1], valid, sig6[0],sig6[1]);
33
34 assign outReal = sig6[0][in_BW+5 : cut_BW]; //added
35 assign outImag = sig6[1][in_BW+5 : cut_BW]; //added
36
```

# Source Codes

## □ Stage.v

```

1  module Stage(nrst,clk,bf_en,cnt,inReal,inImag,valid,outReal,outImag);
2  parameter BW=16;
3  parameter N =32;
4
5  input        nrst,clk,bf_en;
6  input [BW-2:0] inReal,inImag;
7  input [5:0]   cnt;
8  input        valid;
9  output[BW-1:0] outReal,outImag;
10
11 reg [BW-2:0] rReal,rImag;
12
13 wire [BW-1:0] bf_x[1:0];
14 wire [BW-1:0] bf_y[1:0];
15
16 wire [BW-1:0] mult_out[1:0];
17
18 wire [BW-1:0] sr_out[1:0];
19
20 wire [BW-1:0] mux0[1:0];
21 wire [BW-1:0] mux1[1:0];
22
23 assign mux0[0] = bf_en? bf_x[0] : sr_out[0];
24 assign mux0[1] = bf_en? bf_x[1] : sr_out[1];
25
26 assign mux1[0] = bf_en? bf_y[0] : {rReal[BW-2],rReal};
27 assign mux1[1] = bf_en? bf_y[1] : {rImag[BW-2],rImag};
28
29 Shift_Reg #(BW,N) sr0(nrst,clk,mux1[0],valid,sr_out[0]);
30 Shift_Reg #(BW,N) sr1(nrst,clk,mux1[1],valid,sr_out[1]);
31
32 BF #(BW)bf0({sr_out[0][BW-1],sr_out[0][BW-3:0]},{sr_out[1][BW-1],sr_out[1][BW-3:0]},rReal,rImag,bf_x[0],bf_x[1],bf_y[0],bf_y[1]);
33
34 MULT #(.BW(BW),.N(N))mult0(mux0[0],mux0[1],cnt[4:0],mult_out[0],mult_out[1]);
35
36 assign outReal = bf_en? mux0[0] : mult_out[0];
37 assign outImag = bf_en? mux0[1] : mult_out[1];
38
39
40 always@(posedge clk) begin
41     if(!nrst) begin
42         rReal <= 0;
43         rImag <= 0;
44     end
45     else if(valid) begin
46
47         rReal <= inReal;
48         rImag <= inImag;
49     end
50 end
51 end
52
53 endmodule

```

# Source Codes

## □ Stage6.v

```
module Stage6(nrst,clk,bf_en,inReal,inImag,valid,outReal,outImag);
parameter BW=16;
parameter N =1;

input      nrst,clk,bf_en;
input [BW-2:0] inReal,inImag;
input      valid;
output[BW-1:0] outReal,outImag;

reg  [BW-2:0] rReal,rImag;

wire [BW-1:0] bf_x[1:0];
wire [BW-1:0] bf_y[1:0];

reg  [BW-1:0] sr_out[1:0];


wire [BW-1:0] mux0[1:0];
wire [BW-1:0] mux1[1:0];

assign mux0[0] = bf_en? bf_x[0] : sr_out[0];
assign mux0[1] = bf_en? bf_x[1] : sr_out[1];

assign mux1[0] = bf_en? bf_y[0] : {rReal[BW-2],rReal};
assign mux1[1] = bf_en? bf_y[1] : {rImag[BW-2],rImag};

//////////
//////////      Fill your code here      //////////
//////////


endmodule
```

 

# Source Codes
 
## ❑ BF.v

```
1  module BF (Gr,Gi,Hr,Hi,Xr,Xi,Yr,Yi);
2
3  parameter BW =16;
4
5  input  signed [BW-2:0] Gr,Gi,Hr,Hi;
6  output signed [BW-1:0] Xr,Xi,Yr,Yi;
7
8  assign Xr = Gr+Hr;
9  assign Xi = Gi+Hi;
10 assign Yr = Gr-Hr;
11 assign Yi = Gi-Hi;
12
13 endmodule
```



# Source Codes

## □ Shift\_Reg.v

```
1 module Shift_Reg
2 #1
3     parameter BW=16,
4     parameter N =32
5 ) (
6     input nrst,clk,
7     input [BW-1:0] inData,
8     input valid,
9     output[BW-1:0] outData
10 );
11
12 reg    [BW-1:0] sr[N-1:0];
13 integer i;
14
15 always@(posedge clk)
16     if(!nrst)
17         for(i=1;i<N;i=i+1)
18             sr[i] <= 0;
19     else if (valid) begin
20         for(i=1;i<N;i=i+1)
21             sr[i] <= sr[i-1];
22     end
23
24
25 always@(posedge clk)
26     if(!nrst)
27         sr[0] <= 0;
28     else if (valid) begin
29         sr[0] <= inData;
30     end
31
32 assign outData = sr[N-1];
33
34 endmodule
```

